

ShanghaiTech University
School of Information Science and Technology

EE115A Lab Experiments

Experiment : Non- Ideal Op-Amps

1. Pre-Lab

To make the plots more readable and to save on printer toner, change the background color of your plots to white before printing your plot.

1.1 DC Open Loop Transfer Characteristic

Open loop gain A_0 : _____

Voltage offset $V_{off} \equiv -V_{shift}$: _____

Attach your plot of the DC transfer characteristic to the end of the worksheet. Label it please.

1.2 Nulling the Offset Voltage

Draw the circuit used to null the offset voltage connected to the pin out diagram in the space below.

Why do we use a potentiometer to null the offset voltage?